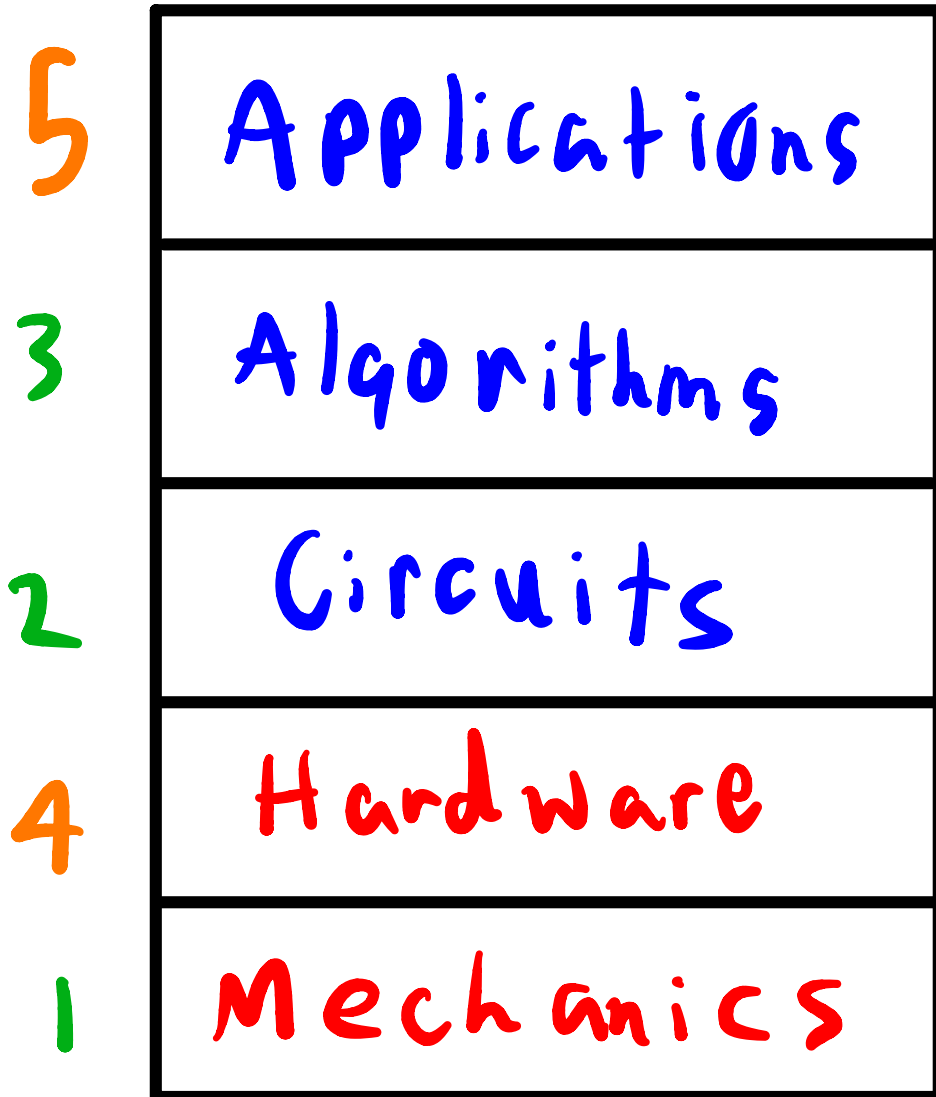




Quantum Circuits III

# The Quantum Computing Stack



Now Getting  
our hands dirty  
w/ circuits  
Last Time  
2+ Qubits

A Quantum Computer

Can do anything a

Classical Computer

can do

# States and Gates

Covered

$$|0\rangle = \begin{bmatrix} 1 \\ 0 \end{bmatrix}$$

$$|1\rangle = \begin{bmatrix} 0 \\ 1 \end{bmatrix}$$

$$|+\rangle = \frac{1}{\sqrt{2}} \begin{bmatrix} 1 \\ 1 \end{bmatrix}$$

$$|-\rangle = \frac{1}{\sqrt{2}} \begin{bmatrix} 1 \\ -1 \end{bmatrix}$$


$$X = \begin{bmatrix} 0 & 1 \\ 1 & 0 \end{bmatrix}$$

$$Y = \begin{bmatrix} 0 & -i \\ i & 0 \end{bmatrix}$$


$$Z = \begin{bmatrix} 1 & 0 \\ 0 & -1 \end{bmatrix}$$

$$H = \frac{1}{\sqrt{2}} \begin{bmatrix} 1 & 1 \\ 1 & -1 \end{bmatrix}$$


# Classical Gates

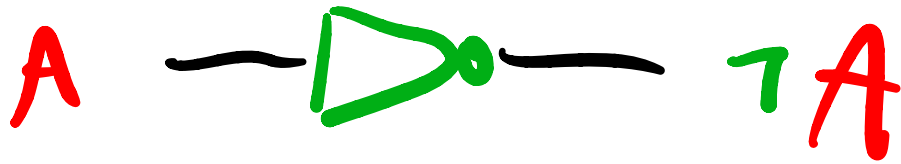


NOT

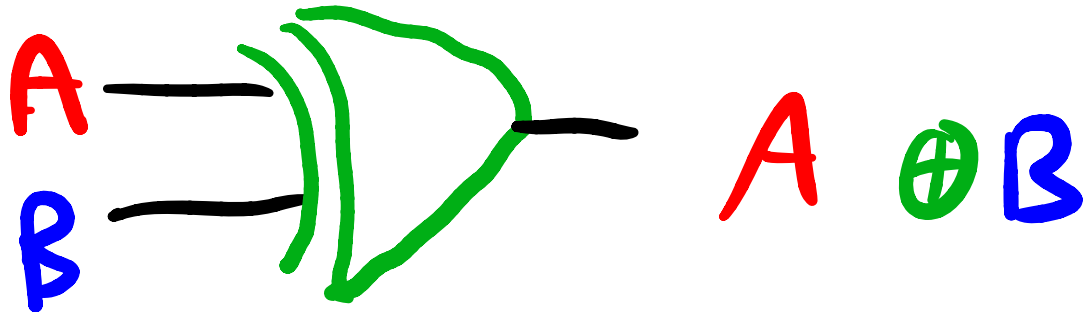

XOR

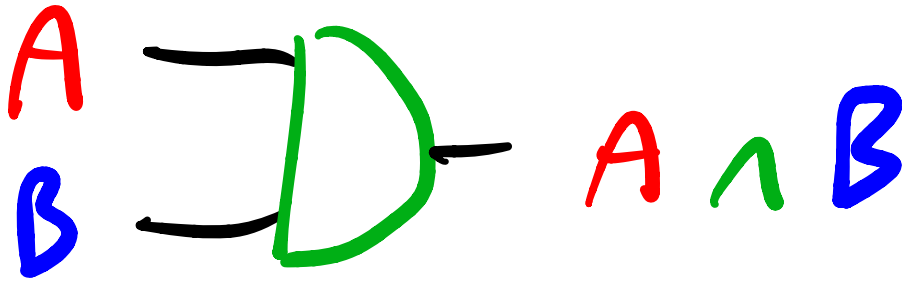


AND

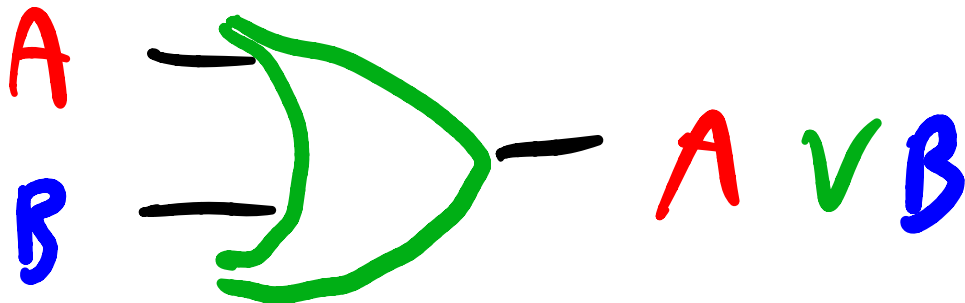

OR

NOT

in	out
0	1
1	0

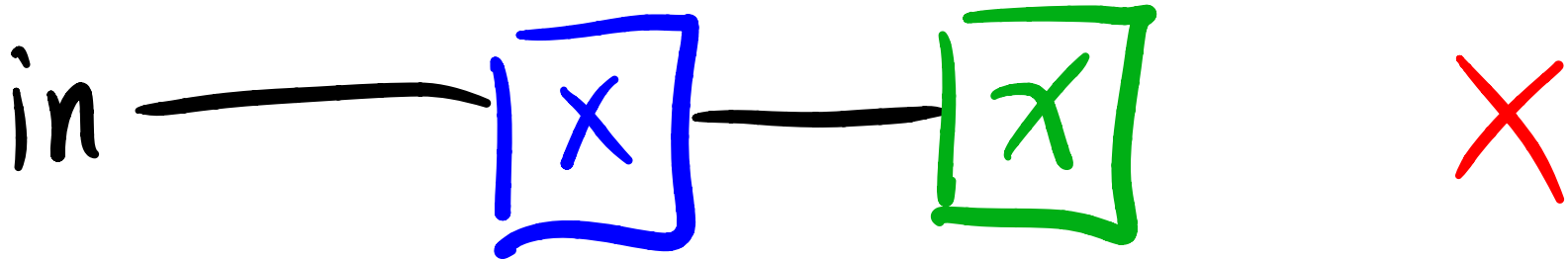

want to separate **in** and **out**

XOR

$in_1$	$in_0$	Out
0	0	0
0	1	1
1	0	1
1	1	0

AND

$in_1$	$in_0$	Out
0	0	0
0	1	0
1	0	0
1	1	1



OR

$in_1$	$in_0$	Out
0	0	0
0	1	1
1	0	1
1	1	1

# Half-Adder

Binary


$in_1$	$in_0$	$out_1$	$out_0$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$in_1 + in_0 = out_1, out_0$$
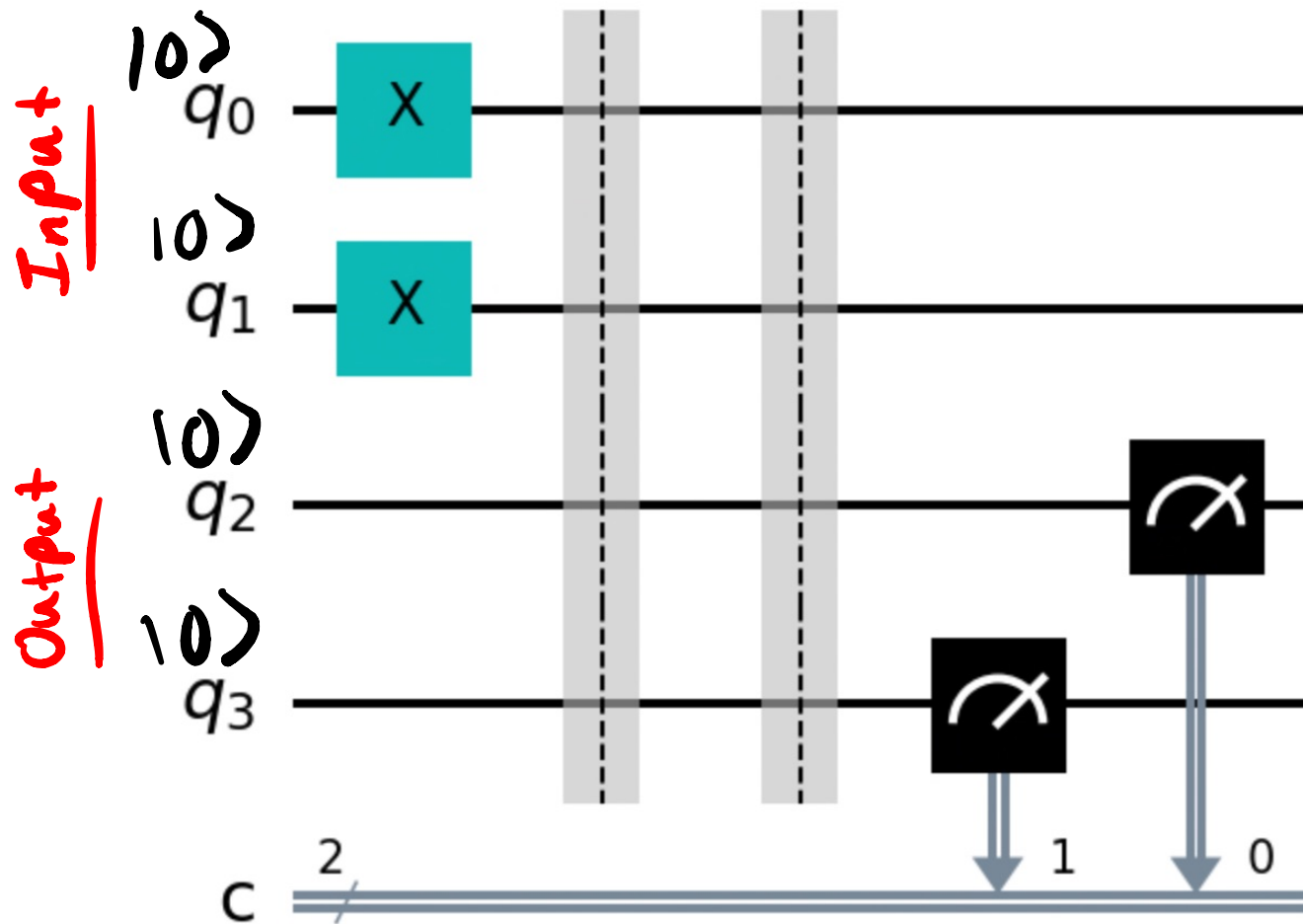
# Half-Adder Skeleton

States      Gates      Measurement

Why are the 'X' gates in the states portion?





Keyword:

Dragon

# Full - Adder

$in_2$	$in_1$	$in_0$	$out_1$	$out_0$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1